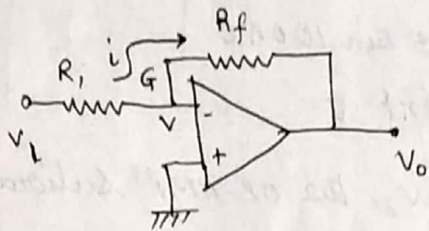


Problems (OPAMP)

(9)

Prob 1: In the inverting amplifier circuit, $R_1 = 1\text{K}\Omega$, and $R_f = 3\text{K}\Omega$. Determine the output voltage, the input resistance and the input current for an input voltage of 2V.




Soln: The output voltage is,

$$V_o = -\left(\frac{R_f}{R_1}\right)V_i = -(3/1) \times 2 = -6\text{V} \quad (\text{Ans})$$

The input resistance $R_{in} = R_1 = 1\text{K}\Omega$

The input current, $i = \frac{V_i}{R_1} = \frac{2}{1}\text{mA} = 2\text{mA}$

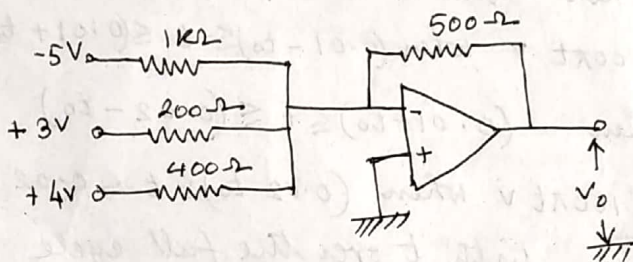Prob 2: Find the output voltage V_o of the three input summing amplifier circuit as in figure below.




Soln: The output voltage should be,

$$V_o = -\left[\frac{500}{1000} \times (-5) + \frac{500}{200} \times 3 + \frac{500}{400} \times 4\right]$$

$$= -(-2.5 + 7.5 + 5) = -10\text{V}$$

$$\therefore \boxed{V_o = 10\text{V}} \quad (\text{Ans})$$

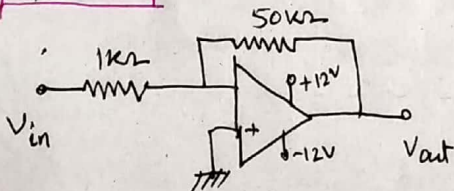Prob 3: Consider the OPAMP circuit as in figure below with a supply voltage of $\pm 12\text{V}$.



Compute the gain and find the output if the input is given as,

$$V_{in} = 0.5 \sin 100\pi t \text{ volt}$$

Soln: Voltage gain of the given inverting amplifier is,

$$A = -\frac{50\text{K}\Omega}{1\text{K}\Omega} = -50$$

If the OP AMP were within linear region over the whole range of input, then the output voltage is,

$$V_{out} = A V_{in} = -50 \times 0.5 \sin 100\pi t$$

$$= -25 \sin 100\pi t \text{ V}$$

Since the supply voltage is $\pm 12\text{V}$, the OP AMP saturates when V_{out} reaches 12V

Let at time $t = t_0$, $V_{out} = -12\text{V}$, Then

$$-12 = -25 \sin 100\pi t_0$$

$$\therefore t_0 = \frac{1}{100\pi} \sin^{-1}\left(\frac{12}{25}\right) = 1.59 \times 10^{-3} \text{ s.}$$

Thus, over the entire cycle we have

$$V_{out} = -25 \sin 100\pi t \text{ V when } 0 \leq t \leq t_0$$


$$= -12\text{V when } t_0 \leq t \leq (0.01 - t_0)$$

$$= -25 \sin 100\pi t \text{ V when } (0.01 - t_0) \leq t \leq (0.01 + t_0)$$


$$= +12\text{V when } (0.01 + t_0) \leq t \leq (0.02 - t_0)$$

$$= -25 \sin 100\pi t \text{ V when } (0.02 - t_0) \leq t \leq 0.02 \text{ s.}$$

The variation of V_{out} with t over the full cycle ($0 \leq t \leq 0.02 \text{ s}$) is shown in figure below.

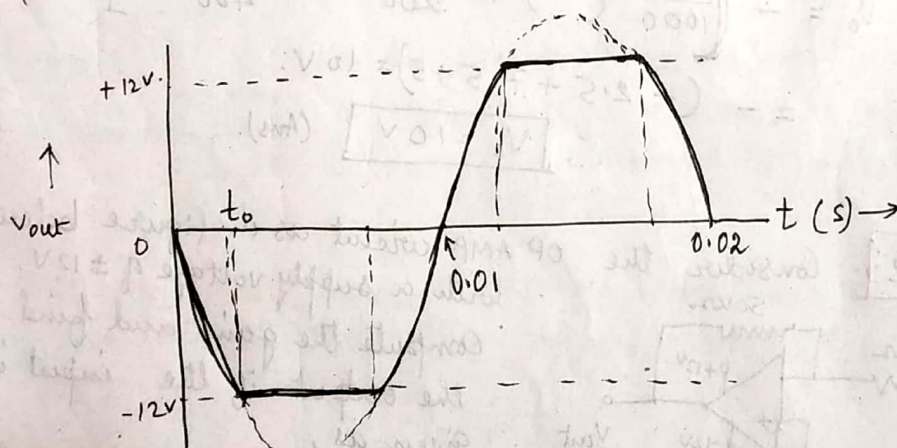

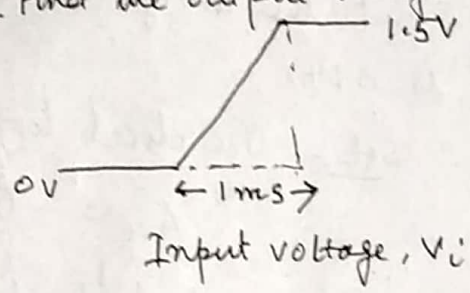Prob 4: A ramp voltage of 1.5V (as shown in fig) per millisecond is applied to an OPAMP differentiator having $R = 2\text{K}\Omega$ and $C = 0.01\mu\text{F}$. Find the output voltage and its waveform.



Soln:

The output voltage is

$$V_o = -RC \frac{dV_i}{dt}$$

Here V_i is shown in figure


For $0 < t < 1\text{ms}$, $\frac{dV_i}{dt} = \frac{1.5\text{V}}{1\text{ms}}$

otherwise, $\frac{dV_i}{dt} = 0$

Also, $RC = 2 \times 0.01 = 0.02\text{ms}$


Hence, $V_o = -0.02 \times 1.5\text{V} = -0.03\text{V} = -30\text{mV}$ for $0 < t < 1\text{ms}$

$V_o = 0$ otherwise

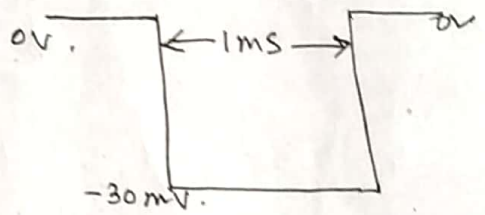

Output voltage, V_o

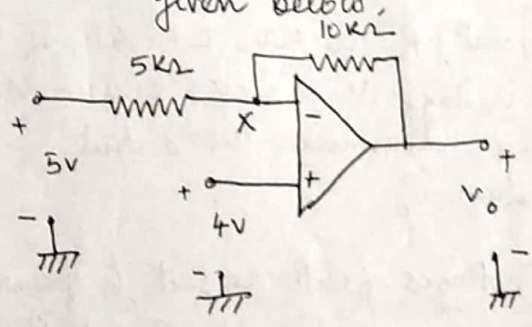Prob 5: Calculate V_o of the circuit given below.



Soln: The gain of the OPAMP being infinite, the potential at the point X in the circuit is 4V. Applying Kirchhoff's current law at X, we obtain

$$\frac{V_o - 4}{10\text{K}\Omega} = \frac{4 - 5}{5\text{K}\Omega}$$

$$\Rightarrow V_o = 2\text{V}$$

(since input impedance of the OPAMP is infinite)

Prob 6: Find the bandwidth of the inverting OP AMP of $R_1 = 1k\Omega$ and $R_2 = 30k\Omega$, Assume that the unity gain bandwidth of the OP AMP is 3 MHz


Soln:- The closed loop gain of inverting OP AMP is

$$A_{vf} = -\frac{R_2}{R_1} = -30$$

Now, $|A_{vf}| \times \text{bandwidth} = \text{Unity gain bandwidth}$

$$\therefore \text{The required bandwidth} = \frac{3 \text{ MHz}}{30} = 100 \text{ kHz}$$

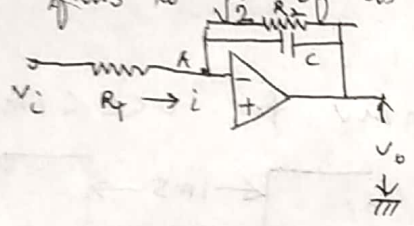Prob 7: Show that in the practical OP AMP integrator circuit below, the frequency at which the voltage gain falls to $\frac{1}{\sqrt{2}}$ of its low frequency value is given by $1/2\pi CR_2$




Soln:
$$\frac{V_o}{V_i} = \frac{R_2 \times \frac{1}{j\omega C}}{R_1(R_2 + \frac{1}{j\omega C})} = \frac{R_2/R_1}{1 + j\omega CR_2}$$

For $\omega = 0$, $\left| \frac{V_o}{V_i} \right| = \frac{R_2}{R_1}$ and

for $\omega CR_2 = 1$, $\left| \frac{V_o}{V_i} \right| = \frac{1}{\sqrt{2}} \frac{R_2}{R_1}$

\therefore The required frequency, $f = \frac{\omega}{2\pi} = 1/2\pi CR_2$

Prob 8:

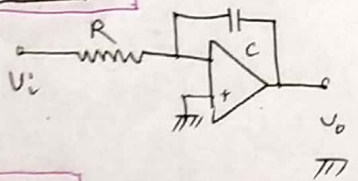


In this circuit $R = 100k\Omega$, $C = 1\mu F$. If the input voltage V_i is $\pm 10V$, 250 Hz square wave, determine the output voltage V_o .

Prob 9:

If V_1 and V_2 are two voltages (with respect to ground), how would you construct an OP AMP circuit to get the voltage $V_o = 2V_1 - V_2$?

Prob 10:

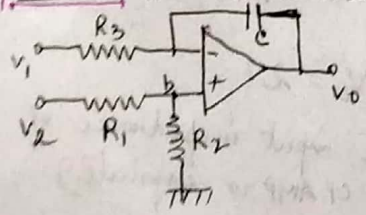

For:- Physics Hons, Sem-4, CE-10
By:- Arpita Bose 26/3/20
Dept. of Physics
Asutosh College