

Subject Name - PHYSICS

Semester - IV

Name of the Teacher - Bidhan Chandra Jana

Name of the Topic - Alternating Currents.

## Alternating Currents

AC Response of a Resistance, an Inductance, and a Capacitance -

### Resistance -

Suppose a voltage  $V(t) = V_0 \sin \omega t$  is applied across a resistance  $R$ . The instantaneous current -

$$i(t) = \frac{V(t)}{R} = \frac{V_0}{R} \sin \omega t = I_0 \sin \omega t$$

where  $I_0 = \frac{V_0}{R}$ .

Here  $i(t)$  is a sinusoidal alternating current with the same frequency as  $V(t)$  and in phase with it.


### Inductance -

Let a sinusoidal current  $i(t) = I_0 \sin \omega t$  pass through an inductance  $L$ . The instantaneous back emf induced across the inductance will be  $-L \frac{di}{dt}$ .

$\therefore$  the voltage across  $L$  is given by

$$\begin{aligned} V(t) &= L \frac{di}{dt} = L \frac{d}{dt} (I_0 \sin \omega t) \\ &= \omega L I_0 \cos \omega t \\ &= \omega L I_0 \sin \left( \omega t + \frac{\pi}{2} \right). \end{aligned}$$

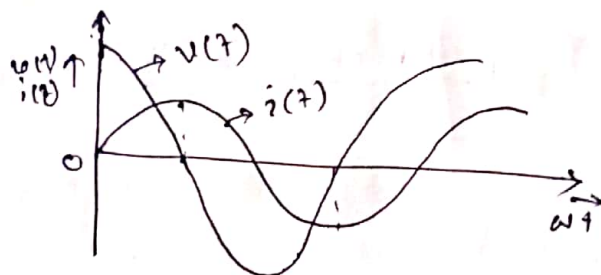$\therefore$  The voltage across an inductance leads the current  $i(t)$  through  $\frac{\pi}{2}$  or  $90^\circ$ .



Variation of  $V(t)$  and  $i(t)$  for the inductance

## Capacitance -

A voltage  $v(t) = v_0 \sin \omega t$  is applied across a capacitor.

The instantaneous charge stored in the capacitor is  $q(t) = C v(t)$

$C$  is the capacitance of the capacitor.


$\therefore$  The instantaneous current in the circuit is -

$$i(t) = \frac{dq}{dt} = C \frac{dv}{dt}$$

$$= \omega C v_0 \cos \omega t$$

$$\Rightarrow i(t) = \omega C v_0 \sin \left( \omega t + \frac{\pi}{2} \right)$$

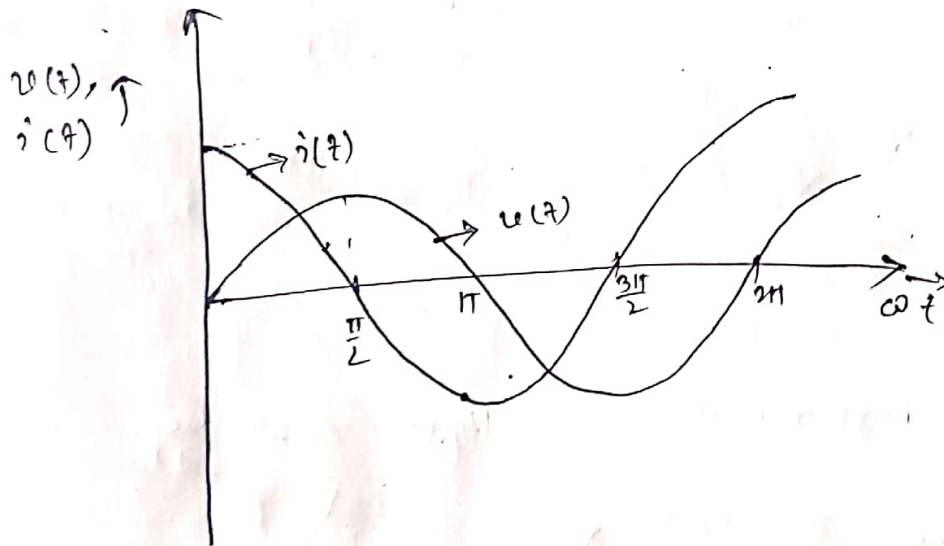$\therefore$  The current  $i(t)$  leads the voltage  $v(t)$  across the capacitor by  $\pi/2$  or  $90^\circ$ .



Variation of  $v(t)$  and  $i(t)$  with  $\omega t$  of the capacitor.

## Root-Mean-Square (RMS) value of current :-

The rms value of a sinusoidal current is, given by  $i(t) = I_0 \sin \omega t$

$$I_{\text{rms}}^2 = \frac{\int_0^T i^2(t) dt}{\int_0^T dt}$$

$$= \frac{I_0^2}{T} \int_0^T \sin^2 \omega t dt$$

$$= \frac{I_0^2}{T} \int_0^T \frac{1 - \cos 2\omega t}{2} dt$$

$$= \frac{I_0^2}{2T} \left[ t - \frac{\sin 2\omega t}{2\omega} \right]_0^T$$

$$= \frac{I_0^2}{2}$$

$$\Rightarrow \boxed{I_{\text{rms}} = \frac{I_0}{\sqrt{2}}}$$

Similarly, rms value of voltage can be

written as

$$\boxed{V_{\text{rms}} = \frac{V_0}{\sqrt{2}}}$$

## Average value of current :-

The average value of a sinusoidal current or voltage over a full cycle is zero. However, it is not zero over a half cycle.

Average for a current  $i(t) = I_0 \sin \omega t$  for a half cycle is given by —

$$I_{av} = \frac{\int_0^{T/2} i(t) dt}{\int_0^{T/2} dt}$$

$$\left| \begin{array}{l} \omega = \frac{2\pi}{T} \\ \omega T = 2\pi \end{array} \right.$$

$$= \frac{2I_0}{T} \int_0^{T/2} \sin \omega t dt$$

$$= \frac{2I_0}{T} \left[ -\frac{\cos \omega t}{\omega} \right]_0^{T/2}$$


$$= \frac{2I_0}{T\omega} \left[ -\cos \frac{\omega T}{2} + \cos 0 \right]$$

$$= \frac{2I_0}{2\pi} [1 + 1]$$

$$\Rightarrow \boxed{I_{av} = \frac{2I_0}{\pi}}$$


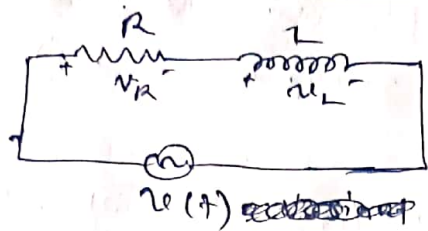
## AC voltage applied to a series LR circuit :-



The emf equation for the circuit is -

$$v_R(t) + v_L(t) = v(t)$$

$$\Rightarrow Ri + L \frac{di}{dt} = v(t)$$

$$\Rightarrow Ri + L \frac{di}{dt} = v_0 e^{j\omega t} \quad \left[ \begin{array}{l} \text{assuming the instantaneous} \\ \text{voltage } v(t) = v_0 e^{j\omega t} \\ * = \operatorname{Re}[v_0 e^{j\omega t}] \end{array} \right] \quad \text{--- (1)}$$

At Steady state current will follow the voltage.

Steady state solution for current can be written as -  $i(t) = I_0 e^{j\omega t}$ ,  $I_0$  is complex quantity.

Now, substituting in eqn (1) -

$$RI_0 e^{j\omega t} + L \frac{d(I_0 e^{j\omega t})}{dt} = v_0 e^{j\omega t}$$

$$\Rightarrow RI_0 + j\omega LI_0 = v_0$$

$$\Rightarrow I_0 = \frac{v_0}{R + j\omega L} = \frac{v_0}{Z}$$

$Z = R + j\omega L$  is known as impedance of the circuit.

$$|Z| = \sqrt{R^2 + \omega^2 L^2}$$


$$\text{and } \tan \theta = \frac{\omega L}{R} ; \theta = \tan^{-1} \left( \frac{\omega L}{R} \right)$$

$$\therefore \text{Impedance, } Z = |Z| e^{j\theta}$$

$\therefore$  The current  $i(t)$  is given by

$$i(t) = \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}} e^{j(\omega t - \theta)}$$

AC applied to a series RC circuit —

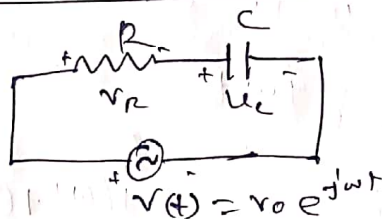

The emf equation for the circuit is —

$$V_R(t) + V_C(t) = V(t).$$

$$\Rightarrow Ri + \frac{q}{C} = V_0 e^{j\omega t} \quad \text{--- (1)} \quad \left| \begin{array}{l} i = \frac{dq}{dt} \\ q = \int i dt \end{array} \right.$$

At Steady State, the current in the circuit can be written as  $i(t) = I_0 e^{j\omega t}$ .  
 $I_0$  is complex.

$\therefore$  From eqn (1), substituting  $i(t)$ .

$$R I_0 e^{j\omega t} + \frac{1}{C} \int I_0 e^{j\omega t} dt = V_0 e^{j\omega t}$$

$$\Rightarrow R I_0 e^{j\omega t} + \frac{I_0}{C} \frac{e^{j\omega t}}{j\omega} = V_0 e^{j\omega t}$$

$$\Rightarrow I_0 = \frac{V_0}{R + \frac{1}{j\omega C}} = \frac{V_0}{R - \frac{j}{\omega C}} = \frac{V_0}{Z}$$

Where,  $Z = R - \frac{j}{\omega C}$  is known as impedance of the circuit.

$$|Z| = \sqrt{R^2 + \frac{1}{\omega^2 C^2}}$$

$$\text{and } \tan \theta = -\frac{1}{\omega CR}$$

$$\therefore Z = R - \frac{j}{\omega C} = |Z| e^{-j\theta}$$


$\therefore$  The current in the circuit —

$$i(t) = \frac{V_0}{Z} e^{j\omega t}$$

$$= \frac{V_0}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} e^{j(\omega t + \theta)}$$

$$\Rightarrow i(t) = I_0 e^{j(\omega t + \theta)}$$

AC in a Series LCR Circuit :-

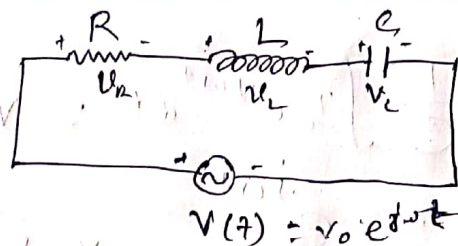

The emf equation for the circuit is

$$V_R(t) + V_L(t) + V_C(t) = V(t)$$

$$\Rightarrow Ri + L \frac{di}{dt} + \frac{q}{C} = V_0 e^{j\omega t} \quad \text{--- (1)}$$

At steady state; the solution for the current is given by  $i(t) = I_0 e^{j\omega t}$ ,  $I_0$  is complex.

From eqn-①, substituting  $i(t)$

$$R I_0 e^{j\omega t} + L I_0 \frac{d}{dt}(e^{j\omega t}) + \frac{1}{C} \frac{I_0 e^{j\omega t}}{j\omega} = v_0 e^{j\omega t} \quad \left[ \because Z = \frac{\int i dt}{i} = \frac{I_0 e^{j\omega t}}{j\omega} \right]$$

$$\Rightarrow R I_0 + j\omega L I_0 + \frac{I_0}{j\omega C} = v_0$$

$$\Rightarrow I_0 = \frac{v_0}{R + j(\omega L - \frac{1}{\omega C})} = \frac{v_0}{Z}$$

Here,  $Z = R + j(\omega L - \frac{1}{\omega C})$  is called impedance of the circuit.

$$|Z| = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$\text{and } \tan \theta = \frac{\omega L - \frac{1}{\omega C}}{R}$$

$$\therefore Z = |Z| e^{j\theta}$$

$\therefore$  The current in the circuit is —

$$i(t) = \frac{v_0}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} e^{j(\omega t - \theta)}$$

### Series Resonance :-

The impedance of the series LCR circuit at an angular frequency  $\omega$  of the applied voltage is

$$Z = R + j(\omega L - \frac{1}{\omega C})$$



at resonance in the circuit, the reactance term must be zero and ~~current~~ current ( $I_0$ ) becomes maximum.

$$\therefore \omega L - \frac{1}{\omega C} = 0$$

$$\Rightarrow \omega = \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\therefore f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{LC}}$$

$f_0$  is the resonant frequency.

At resonance, the circuit is purely resistive.

The impedance at resonance is  $R$ , and the maximum value of current becomes,  $I_0 = \frac{V_0}{R}$ .