


Subject name: Physics ; Semester - IV

Name of the teacher: Bidhan Chandra Jana

Name of topic: Transient Response of Circuits

Series RL Circuit

Growth of Current -

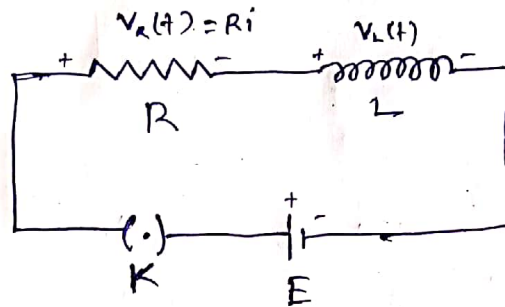

Let  $i(t)$  be the current in the circuit at any time  $t$  after closing the switch  $K$ . The instantaneous induced emf in the coil becomes  $L \frac{di}{dt}$ , and this will oppose the emf  $E$ . The net voltage driving the current  $i$  is  $(E - L \frac{di}{dt})$  and this must be equal to  $Ri$ .

$$\therefore E - L \frac{di}{dt} = Ri$$

$$\Rightarrow L \frac{di}{dt} + Ri = E \quad \dots \dots \textcircled{1}$$

This is the emf equation of the circuit.

Now, from eqn  $\textcircled{1}$

$$L \frac{di}{dt} = E - Ri$$

$$\Rightarrow \frac{di}{E - Ri} = \frac{dt}{L}$$

~~or~~ Integrating,

$$\int_0^i \frac{di}{E - Ri} = \int_0^t \frac{dt}{L} \quad \left( \because \text{at } t=0, i=0 \right)$$

$$\Rightarrow \left[ -\frac{1}{R} \ln(E - Ri) \right]_0^i = \left[ \frac{t}{L} \right]_0^t$$

$$\Rightarrow -\frac{1}{R} [\ln(E - Ri) - \ln(E)] = \frac{t}{L}$$

$$\Rightarrow \ln\left(\frac{E - Ri}{E}\right) = -\frac{Rt}{L}$$

$$\Rightarrow 1 - \frac{R}{E}i = e^{-\frac{Rt}{L}}$$


$$\Rightarrow \boxed{i = \frac{E}{R} (1 - e^{-\frac{Rt}{L}})} \quad \left[ \frac{E}{R} = i_0 = \text{Steady state current} \right]$$

The quantity  $\frac{L}{R}$  has the dimension of time and is called time constant ( $\tau$ ),

$\therefore$  at  $t = \tau$ ,


$$i = \frac{E}{R} 0.63 = 0.63 i_0$$

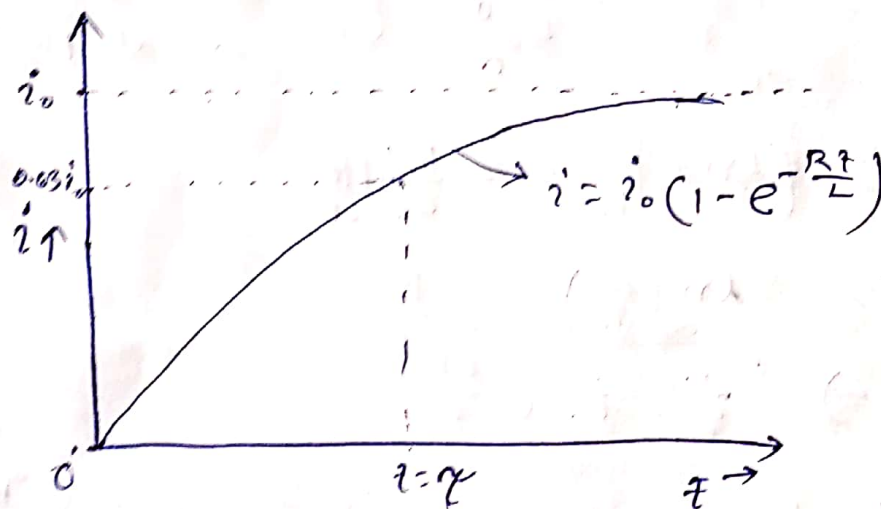$\therefore$  Time required to reach the 63 percent of its maximum value is time constant of the circuit.



Growth of current in RL circuit

# Delay of current

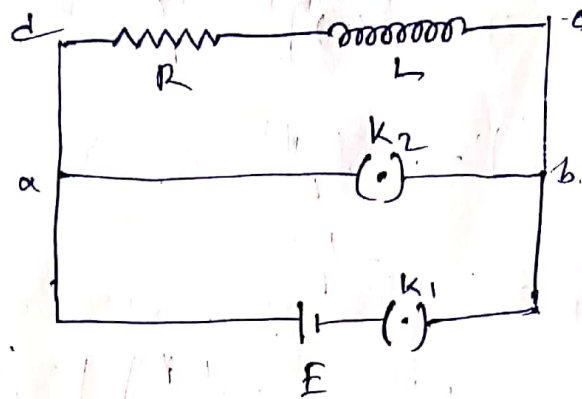

Once the circuit ~~at~~ reached to the steady state, at time  $t=0$  the switch  $K_1$  is opened and simultaneously the switch  $K_2$  is closed. In the closed circuit  $abcd$ , the driving emf is zero,

now, if  $i(t)$  is the current at time  $t$  in the  $abcd$ , then

$$L \frac{di}{dt} + Ri = 0$$

$$\Rightarrow \frac{di}{i} = -\frac{R}{L} dt$$


$$\Rightarrow \int_{i_0}^i \frac{di}{i} = -\frac{R}{L} \int_0^t dt \quad \left[ \because \text{at } t=0, i=i_0 \text{ and at time } t, \text{ current is } i \right]$$

$$\Rightarrow [\ln i]_{i_0}^i = -\frac{R}{L} [t]_0^t$$

$$\Rightarrow \ln \left( \frac{i}{i_0} \right) = -\frac{Rt}{L}$$


$$\Rightarrow \boxed{i = i_0 e^{-\frac{Rt}{L}}}$$

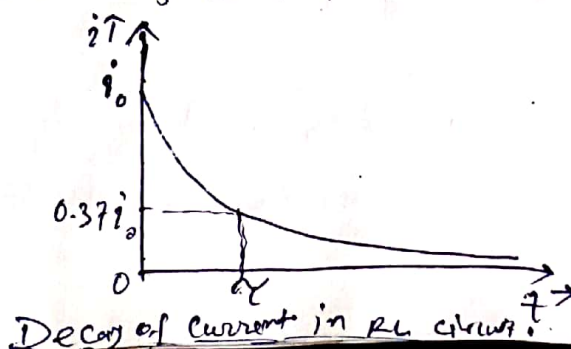Hence the time constant  $\frac{L}{R}$  is the time taken by the current to decay 37 percent of its initial value.



# Series RC Circuit

## Charging of the Capacitor

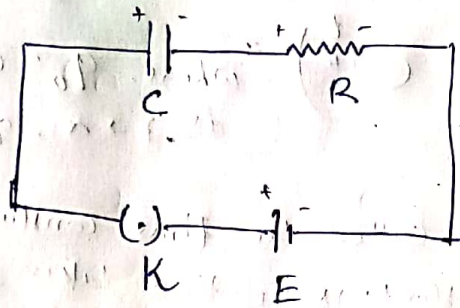

Let, at any instant of time  $t$ , the voltage across the capacitor be  $V_c(t)$  and that across the resistance be  $V_R(t)$

The emf equation for the circuit is

$$V_c(t) + V_R(t) = E \quad \text{--- (1)}$$

Since,  $i = \frac{dq}{dt}$  and  $q = CV_c$  = charges stored on the capacitor at time  $t$ ,

$$\therefore V_c(t) = \frac{q}{C} \quad \text{and} \quad V_R(t) = Ri = R \frac{dq}{dt}$$

From eqn (1) —

$$\frac{q}{C} + R \frac{dq}{dt} = E$$

$$\Rightarrow \frac{dq}{E - \frac{q}{C}} = \frac{dt}{R}$$

Integrating —

$$\int_0^q \frac{dq}{E - \frac{q}{C}} = \int_0^t \frac{dt}{R}$$

$$\Rightarrow \left[ -C \ln \left( E - \frac{q}{C} \right) \right]_0^q = \frac{1}{R} [t]_0^t$$

$$\Rightarrow \ln \left( E - \frac{q}{C} \right) - \ln(E) = -\frac{t}{CR}$$

$$\Rightarrow \ln \left( \frac{E - \frac{q}{C}}{E} \right) = -\frac{t}{CR}$$




$$\Rightarrow 1 - \frac{q}{cE} = e^{-\frac{t}{CR}}$$


$$\Rightarrow q = cE(1 - e^{-\frac{t}{CR}})$$

$$\Rightarrow q = q_0(1 - e^{-\frac{t}{CR}}) \left[ \text{where, } q_0 = cE \right. \\ \left. \text{as } t \rightarrow \infty, q = q_0 \right]$$

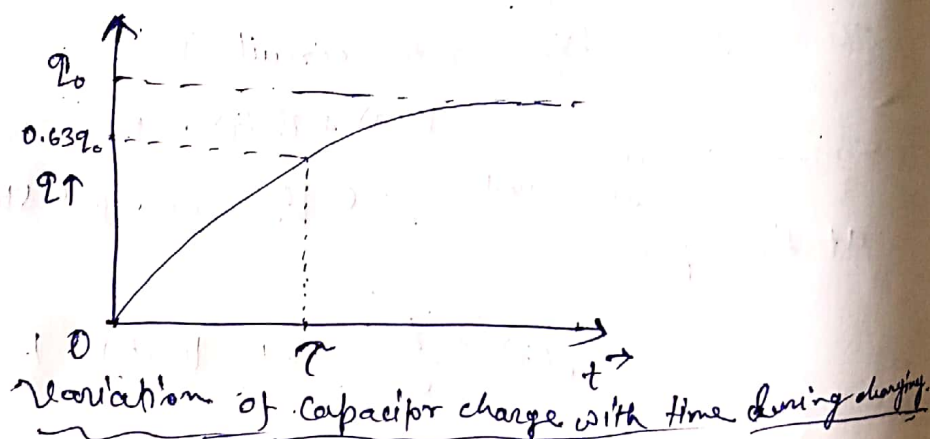Here, the quantity  $CR$  is called the time constant  $\tau$  of the circuit. The time constant is the time taken for a capacitor to acquire 63 percent of its final maximum charge.



### Discharging of the capacitor —

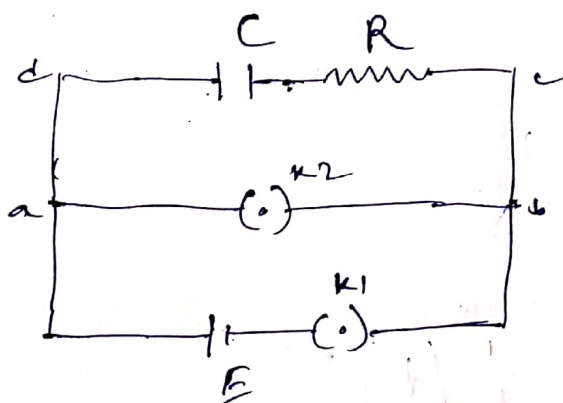

Once the capacitor is fully charged to  $q_0$ , the switch  $K_1$  is opened and  $K_2$  is closed simultaneously.

In the closed path abcd, the induced emf is zero. So the emf equation is

$$\frac{q}{C} + R \frac{dq}{dt} = 0$$

$$\Rightarrow \frac{dq}{q} = - \frac{dt}{CR}$$


Integrating —

$$\int_{q_0}^q \frac{dq}{q} = - \frac{1}{CR} \int_0^t dt \quad \left[ \because \text{at } t=0, q=q_0 \right]$$

$$\Rightarrow [\ln q]_{q_0}^q = - \frac{1}{CR} [t]_0^t$$

$$\Rightarrow \ln \frac{q}{q_0} = - \frac{t}{CR}$$
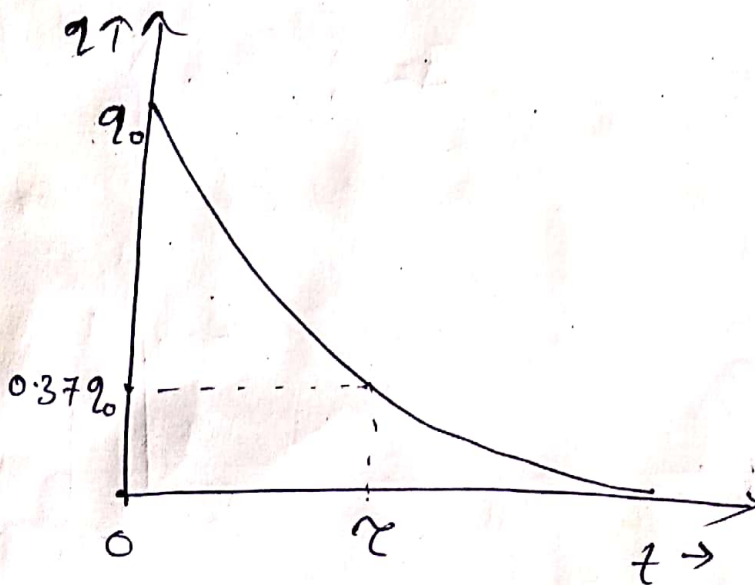
$$\Rightarrow \boxed{q = q_0 e^{-\frac{t}{CR}}}$$



Decay of capacitor charge with time.